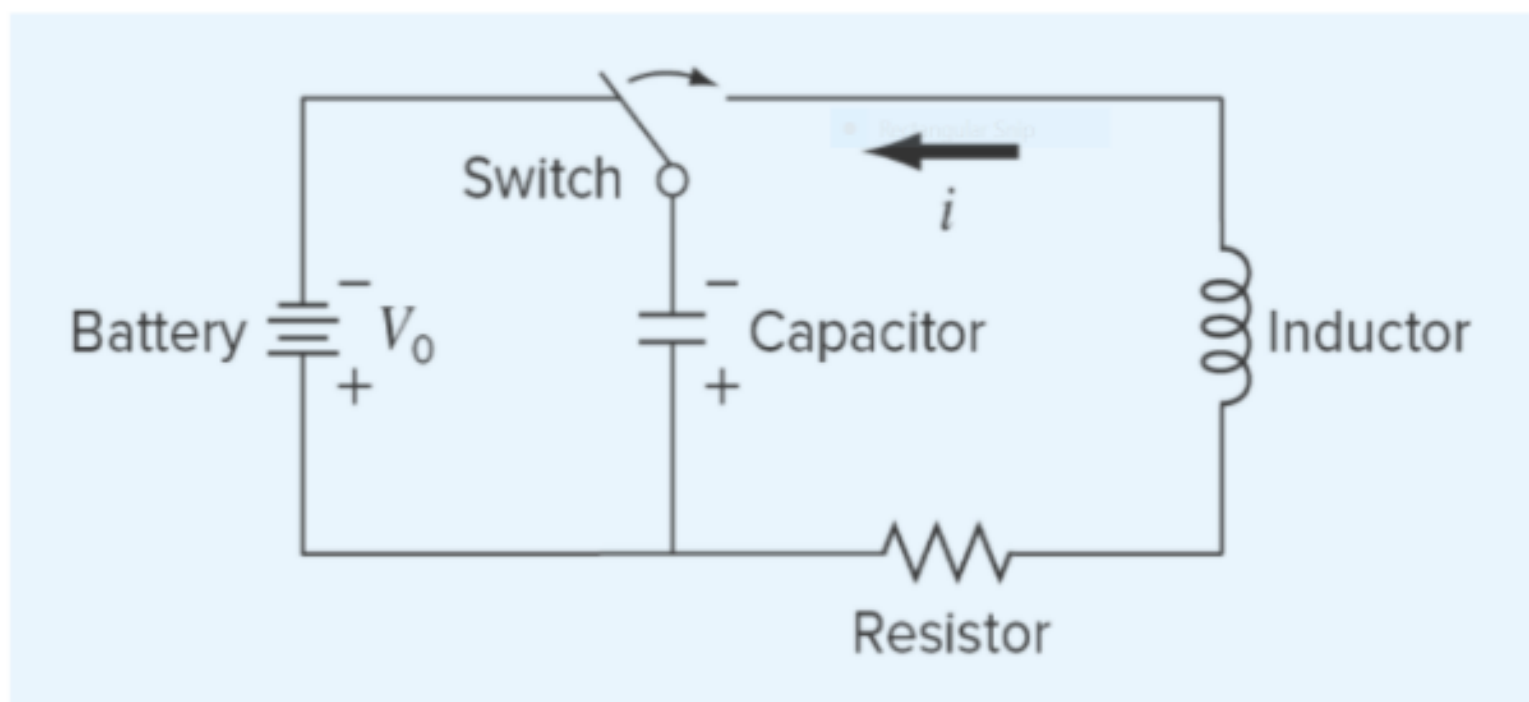


Problem 1: Simple Electrical Circuit

1 solution submitted (max: Unlimited) | [View my solutions](#)

Consider a simple electric circuit consisting of a resistor, a capacitor, and an inductor as shown below



The charge on the capacitor $q(t)$ as a function of time can be computed as:

$$q(t) = q_0 e^{-Rt/2L} \cos \left(\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2} t \right)$$

where:

t = time

q_0 = initial charge

R = the resistance

L = inductance

C = capacitance